
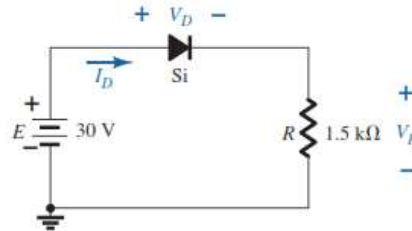

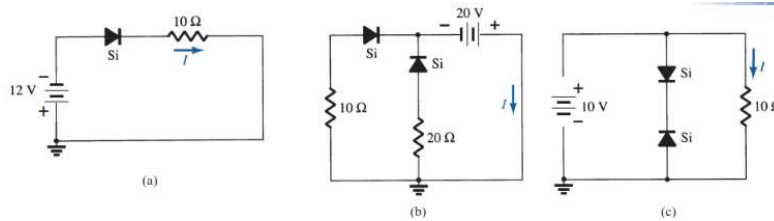
## Sheet (2) Diodes Applications


- Using the approximate characteristics for the Si diode, determine  $V_D$ ,  $I_D$ , and  $V_R$  for the circuit of fig. below:
  - Perform the same analysis as part (a) using the ideal model for the diode.
  - Do the results obtained in parts (a) and (b) suggest that the ideal model can provide a good approximation for the actual response under some conditions?














- Determine the current  $I$  for each of the configurations of Fig. below using the approximate equivalent model for the diode.



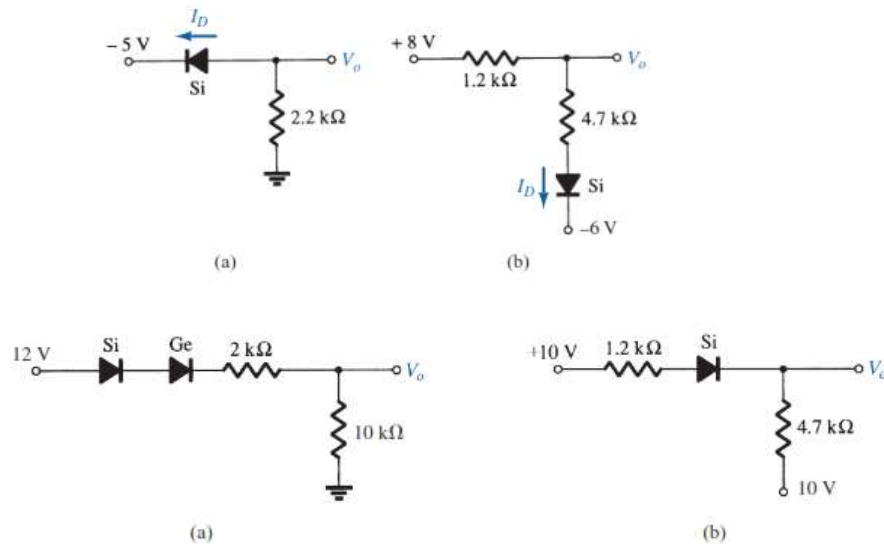
- Determine  $V_o$  and  $I_D$  for the networks of Figs. below



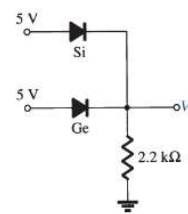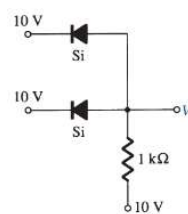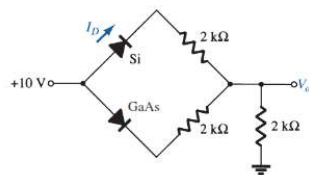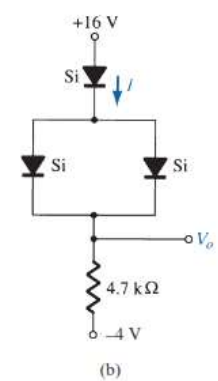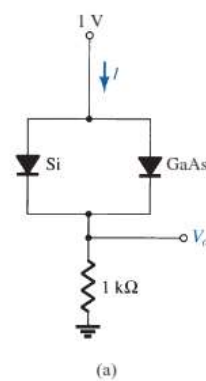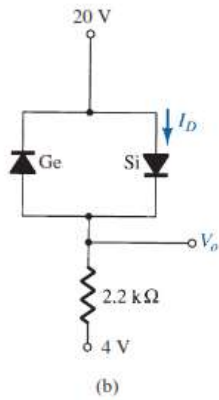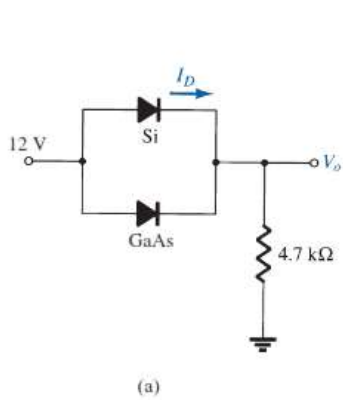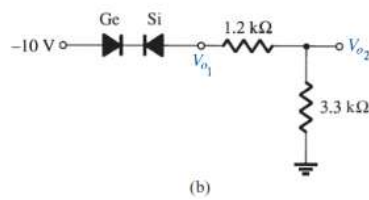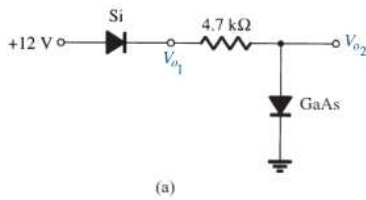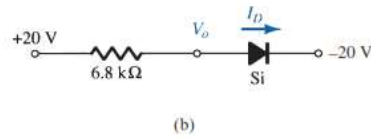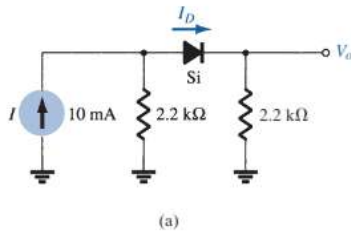
4. Determine  $V_o$  and  $I_D$  for the networks of Figs. below (some Figs. find  $V_{o1}$   $V_{o2}$ )



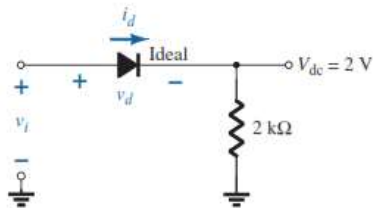
5. Assuming an ideal diode, sketch  $v_i$ ,  $v_d$ , and  $i_d$  for the half-wave rectifier of Fig. The input is a sinusoidal waveform with a frequency of 60 Hz. Determine the peak value of  $v_i$  from the given dc level.
- Repeat with a silicon diode ( $V_K = 0.7$  V).



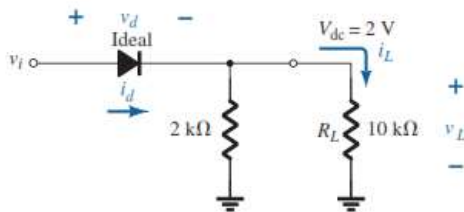
6. Repeat with a 10 kohm load applied as shown in Fig. Sketch  $v_L$  and  $i_L$



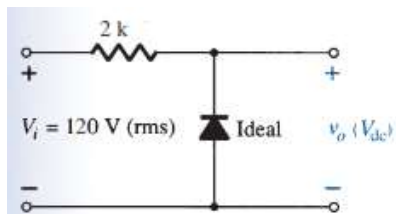
7. For the shown figures find remarked quantities.



8. Sketch  $v_o$  and  $i_R$

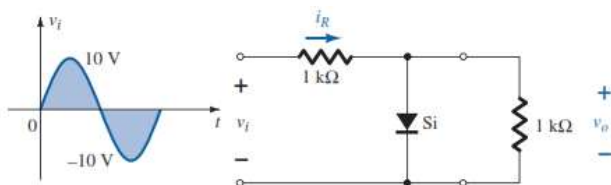


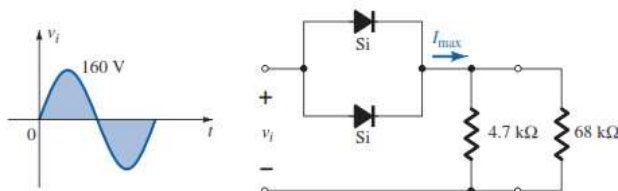9. Given  $P_{\max} = 14 \text{ mW}$  for each diode at Fig. below, determine the maximum current rating of each diode (using the approximate equivalent model).
- Determine  $I_{\max}$  for the parallel diodes.
  - Determine the current through each diode at  $V$  using the results of part (b).
  - If only one diode were present, which would be the expected result?




10. A full-wave bridge rectifier with a 120-V rms sinusoidal input has a load resistor of 1kohm.
- If silicon diodes are employed, what is the dc voltage available at the load?
  - Determine the required PIV rating of each diode.
  - Find the maximum current through each diode during conduction.
  - What is the required power rating of each diode?

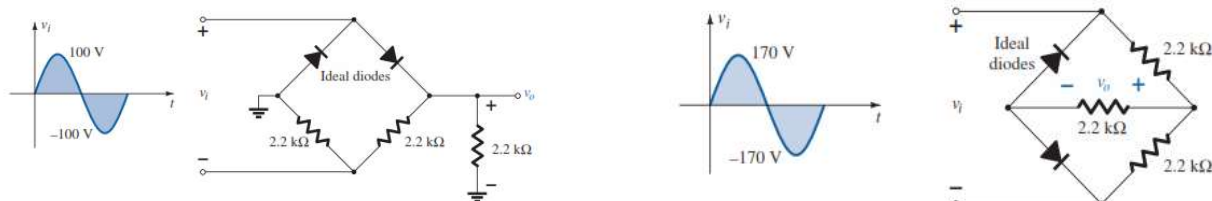
11. Sketch  $v_o$  for the network of Figure below and determine the dc voltage available.



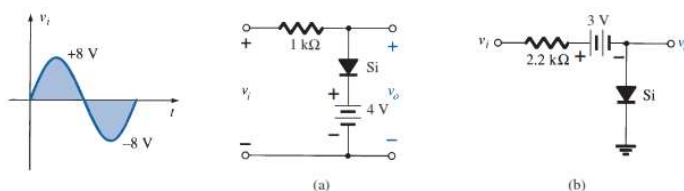12. Determine  $v_o$  for each network of Figure below for the input shown.



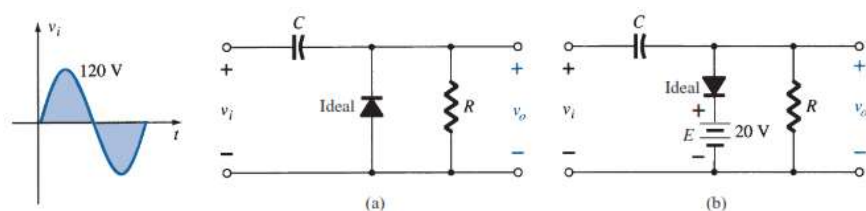13. Sketch  $v_o$  for each network of Figure below for the input shown.



14. a. Determine  $V_L$ ,  $I_L$ ,  $I_Z$ , and  $I_R$  for the network of Figure below if  $R_L=180\ \Omega$   
b. Repeat part (a) if  $R_L = 470\ \Omega$ .  
c. Determine the value of  $R_L$  that will establish maximum power conditions for the Zener diode.  
d. Determine the minimum value of  $R_L$  to ensure that the Zener diode is in the “on” state.

